

CAP48: Disconnection Triggers







Steve Curtis




CAP48: Disconnection Triggers

- A number of transmission system outages / faults could lead to the disconnection of generation
- It is often difficult to determine the circumstances for which CAP48 payments are applicable
- The following slides show a number of potential disconnection triggers
- Is CAP48 applicable?



THE POWER OF ACTION

Bar outage: intact double bus station

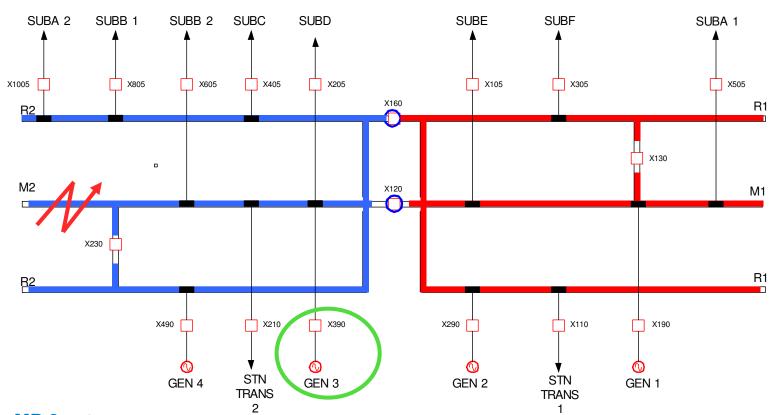

Assume MB 2 outage:

Unplanned:

Main Bar 2 Fault
Generator 3 disconnected
Will be off until transfer to B2


Planned:

Would reselect ccts and generators prior to outage to prevent disconnection.....



THE POWER OF ACTION.

Bar outage: depleted double bus station

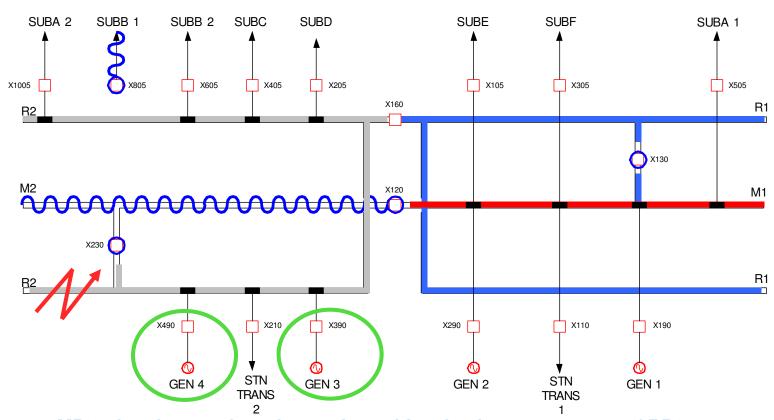

Now assume MB 2 already out of service, and consider simultaneous outage of RB2:

Unplanned:


Main Bar 2 out of service Reserve Bar 2 Fault Generator 3 and 4 disconnected Will be off until R2 or M2 restored

Planned:

Main Bar 2 out of service Reserve Bar 2 would not normally be expected to be planned at same time (but could be)



Depletion of Station Supplies

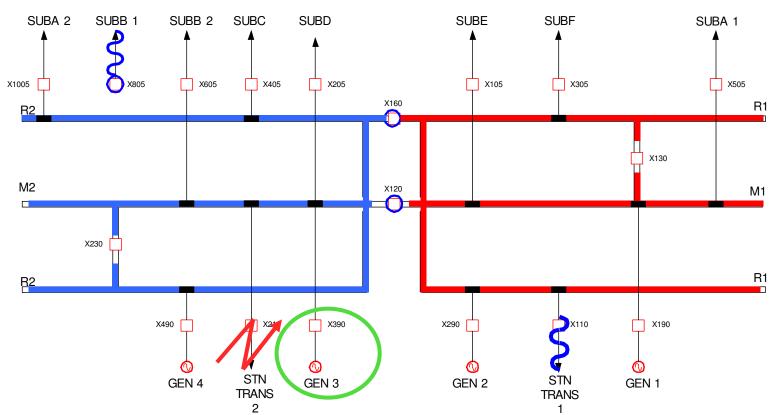

Assume Station Transformer 1 out of service and consider simultaneous outage of Station Transformer 2:

Unplanned:


Power station supplies disconnected All units will desynchronise (non instantaneous)? Re-synch after restoration of supplies

Planned:

Would not plan simultaneous outages of both Transformers



Local circuit outages

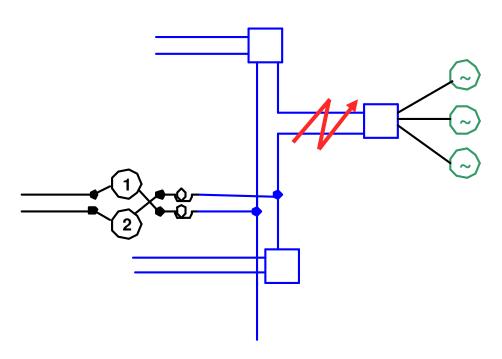

Assume loss of double circuit connecting power station to system

Unplanned:


Power station disconnected Often covered (but not always) by CAP76 Cat 4 intertrip (paid under CAP76 terms) Re-connection on restoration of one or more circuits

Planned:

Would not normally plan simultaneous outages of both circuits
NB some single circuit connections, **most** covered by BCA



Remote circuit outages

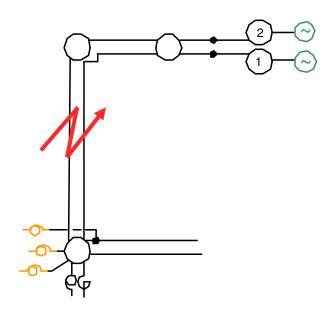

Assume loss of double circuit connecting power station to system

Unplanned:

Power station disconnected


Planned:

Would not **normally** plan simultaneous outages of both circuits



Wider outages



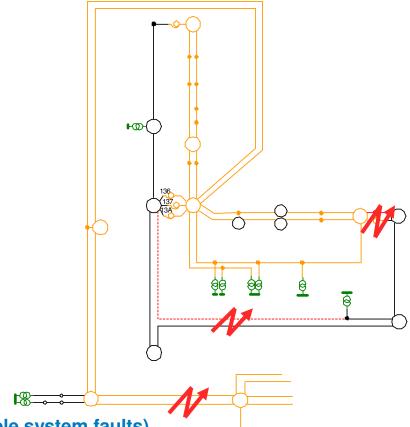

Assume wider losses (e.g. multiple system faults)

Unplanned:

Multiple faults disconnect part of transmission system. Power island not viable; a number of power stations disconnected (perhaps instantaneously, perhaps after delay)

Planned:

N/A



Other

Disconnection following fault in proximity(eg Stability / Low Frequency / ROCOF) ?

Switching Error ?

Specific supplies (eg dedicated FGD supplies; could be considered akin to station supplies)?